

University of Bedfordshire

Unit Code: CIS108-2
Unit Title Dynamics, Measurements and Control
Academic Year 2021/22
Period of Study **SEM 1 Paper 1**

Time Allowed: 2 HOURS

Unit Co-Ordinator: Dr Mina Mortazavi

Instructions for Candidates

Do not open this paper until instructed to do so by the Senior invigilator

Equipment allowed: Basic, non-programmable Calculator

Materials allowed: *None*

Materials supplied *Formula sheet supplied*

Additional Instructions: Type of Exam:
This is a closed book examination

There are TWO sections:

Answer All questions from section A and THREE out of FOUR questions from Section B

Section A: SHORT ANSWER QUESTIONS

-
- *Answer All Questions in SECTION A*
- *Each question carries 5 marks*

Question 1

Find the equivalent resistor (R_{total}) for the network presented in Figure 1A.

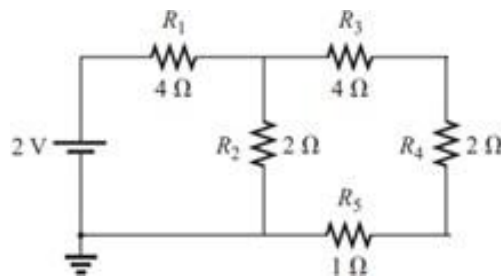


Figure 1A


[5 Marks]

Ans;
Equation R

$$\begin{aligned}
 &= R_3 + R_4 + R_5 \\
 &= 4 + 2 + 1 \\
 &= 7
 \end{aligned}$$

$$\begin{aligned}
 R_{eq} &= R_2 + R_{eq} \\
 &= \frac{1}{2} + \frac{1}{7} \\
 &= \frac{9}{14} \\
 &= 0.64
 \end{aligned}$$

$$\begin{aligned}
 R_{eq} &= \frac{9}{14} + 4 \\
 &= \frac{9 + 56}{14} \\
 &= \frac{65}{14} \\
 R_{eq} &= 4.64
 \end{aligned}$$

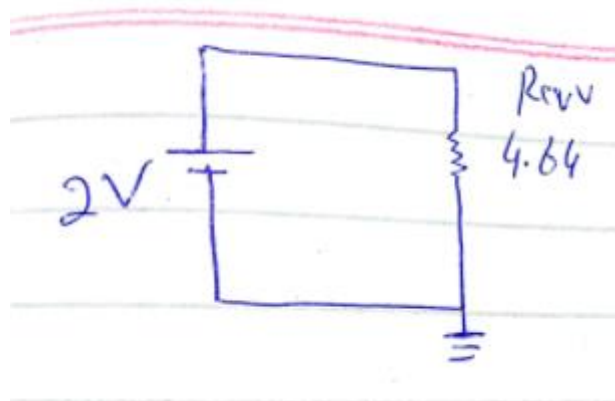

Question 2

You have been given a task to select a sensor; name four different selection criteria for your sensor selection, briefly explain two of them.

[5 Marks]

Ans;


1. Temperature
2. Size
3. Protection Glass
4. Discrete or analog input

Question 3

Using a simple diagram, briefly explain the speed- torque relation for a DC motor.

[5 Marks]

Ans;

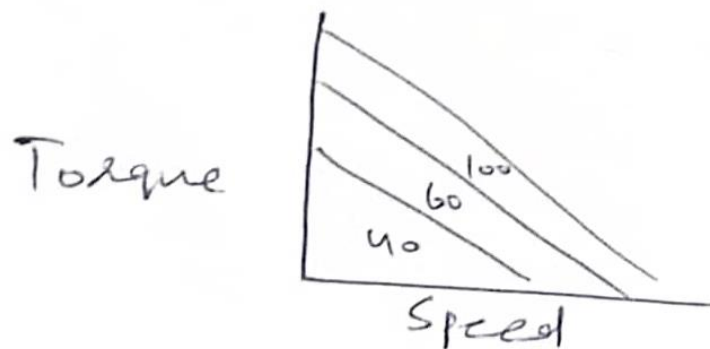


DC motors are relatively simple machines.

When supply voltage is constant, the Torque T is inversely proportional to speed W .

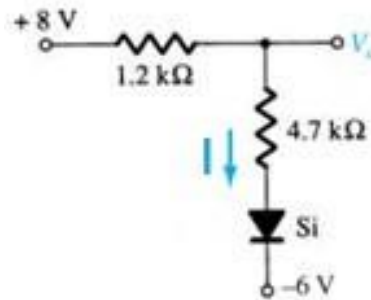Question 4

For the circuit presented in Figure 2A, find the current I and V_o , if the diode is a silicon type
($V_D = 0.7 \text{ volts}$)



[5 Marks]

Ans;

$$\begin{aligned} V_d &= 0.7V \\ I &= \frac{V_1 R_1 - V_2 R_2}{R_1 R_2} \\ &= \frac{8 \times 1.2 - 4.7 \times 0.7}{1.2 \times 4.7} \\ &= \frac{9.6 - 3.29}{5.64} \\ &= 0.413 \\ V &= V_{in} - V_g \\ &= 8 - 6 \\ \mathbf{V} &= \mathbf{2V} \end{aligned}$$

Question 5

Overall transfer function for a control system is given by: $T(s) = \frac{3}{s^2 + 8s + 3}$.

Considering the damping factor, which type of the system, this transfer function demonstrates?

[5 Marks]

Ans:


$$\begin{aligned} T(s) &= \frac{3}{s^2 + 8s + 3} \\ T(s) &= \frac{8}{2} = 4 \\ \mathbf{T(s)} &= \mathbf{4 > 1} \\ \mathbf{So overdamped} \end{aligned}$$

Section B: LONG ANSWER QUESTIONS

- Answer any 3 (THREE) questions only.
- Each question carries 25 marks.

Question 1

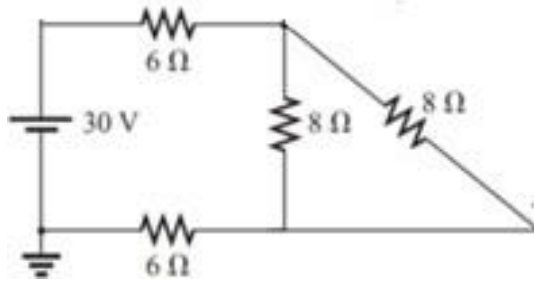a) Find the total current and the total power dissipated in circuit of Figure 1B.



[12 Marks]

Ans:

$$V = 30V$$

$$R = \frac{8 \times 8}{8 + 8}$$

$$= \frac{64}{16} = 4$$

$$= 4 + 6 + 6$$

$$= 16$$

$$RI = V$$

$$I = \frac{V}{R}$$

$$= \frac{30}{16}$$

$$= 1.87$$

$$\text{Power} = V^2 I$$

$$= (30)^2 \times 1.87$$

$$= 1687.5 W$$

b) Figure 2B presents a bridge circuit to measure the temperature. If R_{sensor} is 650Ω , calculate the V_{output} .

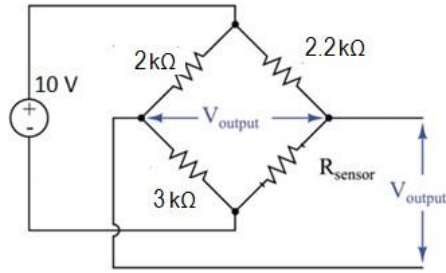



Figure 2B

[5 Marks]

(b)

$$\begin{aligned}
 R_x &= \frac{2.2}{2+3} \\
 &= \frac{2.2}{5} \\
 &= \frac{2.2}{5} \times 650 \\
 &= 650/250 \\
 V_{out} &= 16V
 \end{aligned}$$

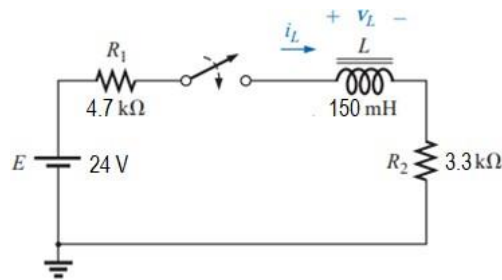- c) For the network of Figure 3B,
- write the mathematical expressions for the current i_L and the voltage V_L following the closing of the switch.
 - How long does it take for the i_L to reach its maximum level?



[8 Marks]

$$k) \text{ (i) } di = L \frac{dv}{dt}$$

$$\text{(ii) } L = 150 - 3.3$$

$$= 146.7$$

Question 2

- a) Find the equivalent capacitor between terminal **A** and **B** in Figure 4B. If a voltage of 40 V is applied across the terminal **AB**, calculate the energy stored in equivalent capacitor in Joules.

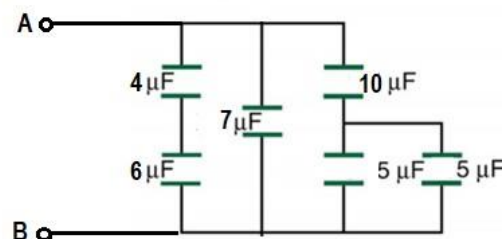


Figure 4B

$$\begin{aligned}
 P) & \\
 &= 5+5 \\
 &= 10 \\
 &= \frac{10 \times 10}{10+10} \\
 &= \frac{100}{20} \\
 &= 5+7 \\
 &= 12 + 6114 \\
 &= 12 + \frac{6 \times 9}{6+4} \\
 &= 12 + \frac{24}{10} \\
 &= 12 + 2.4 \\
 C &= 144 \\
 Q &= CV \\
 E &= 14.4 \times 40 \\
 &= 576
 \end{aligned}$$

b)

The combinational logic system presented in Figure 5B, accepts 2-bit binary numbers. Complete the Truth table below for this system.

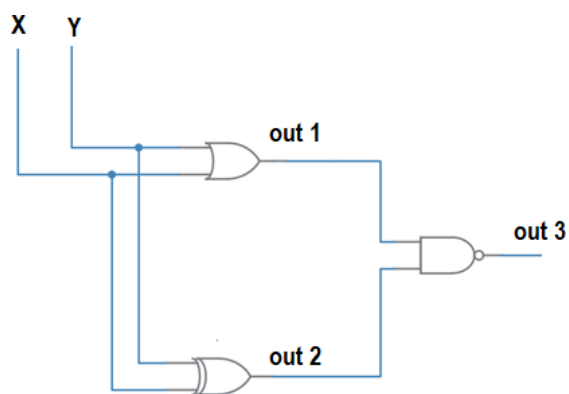


Figure 5B

X	Y	Out 1	Out 2	Out 3
0	0			


0	1			
1	0			
1	1			

(b)


X	Y	out 1	out 2	out 3
0	0	0	1	1
0	↓	0	1	1
1	0	0	1	1
1	1	1	0	1

Question 4

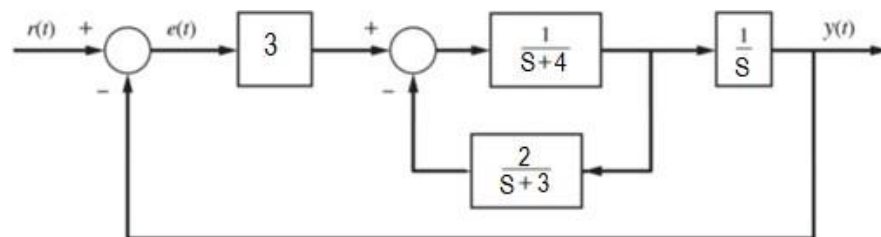
a) Find the close loop transfer function for the system presented in Figure 7B.



[10 Marks]

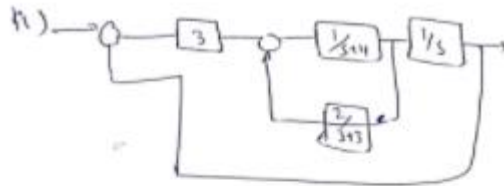

$\frac{1}{s+4}$ and $\frac{2}{s+3}$ are ||

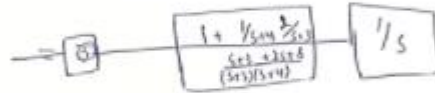

Now all are in series

$$= 3 + 1 + \frac{(1/(s+4)) (2/(s+3))}{\frac{3s+1}{(s+3)(s+4)}} + 1/s$$

$$= 3 + \frac{1 + \frac{2}{3s+1}}{3s+1} + 1/s$$

$$= 3 + \frac{4}{3s+1} + 1/s$$

$$= \frac{9s + 3 + 4 + 2s + 1}{3s + 1}$$

$$= \frac{11s + 9}{3s + 1}$$

- b) Using Routh-Hurwitz method, determine if the control system presented in Figure 7B is stable or not. Why?

[8 Marks]

Routh-Hurwitz method, so its not stable.

c) Using a general diagram, present main components of a pneumatic actuator.

[7 Marks]

T-domain	S-domain	T-domain	S-domain
1	$\frac{1}{s}$	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
t	$\frac{1}{s^2}$	$e^{-at} \sin \omega t$	$\frac{\omega}{(s + a)^2 + \omega^2}$
e^{-at}	$\frac{1}{s + a}$	$e^{-at} \cos \omega t$	$\frac{s + a}{(s + a)^2 + \omega^2}$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$	$\frac{df(t)}{dt}$	$sF(s) - f(0)$

Formula Sheet

$$U = \frac{1}{2}CV^2$$

$$\epsilon\epsilon_0 = 8.854 \times 10^{-12}$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$